

# DIGITAL SYSTEM DESIGN

## EC-503

BY

DR. GAURAV KUMAR BHARTI

ASSISTANT PROFESSOR

DEPT. OF ELECTRONICS & COMMUNICATION ENGINEERING  
INDIAN INSTITUTE OF INFORMATION TECHNOLOGY BHOPAL,

# REVIEW OF SEQUENTIAL CIRCUITS

# COMBINATIONAL VS SEQUENTIAL

## Combinational

- Combinational circuits generate output solely based on the current inputs.
- These circuits have no internal memory elements to store past inputs or outputs.
- Output depends only on the present combination of inputs.
- Output changes instantly with any change in input.
- All outputs are available simultaneously.
- **Examples :**
  - **Logic Gates:** Basic building blocks like AND, OR, NOT.
  - **Multiplexers, Demultiplexers:** Devices that perform operations based on input combinations.

## Sequential

- Sequential circuits include memory elements (usually flip-flops) to store past inputs and outputs.
- Output not only depends on current inputs but also on the circuit's past states.
- Utilizes feedback to retain information.
- Synchronized operation with a clock signal.
- Outputs are generated sequentially, one after another.
- **Examples :**
  - **Registers:** Used for data storage in CPUs.
  - **Counters:** Sequential circuits that count or generate sequences.
  - **Memory Units:** Store information for later retrieval.

# Combinational and sequential circuits

- The Fig1 and Fig2 shows the pictorial representation of circuits

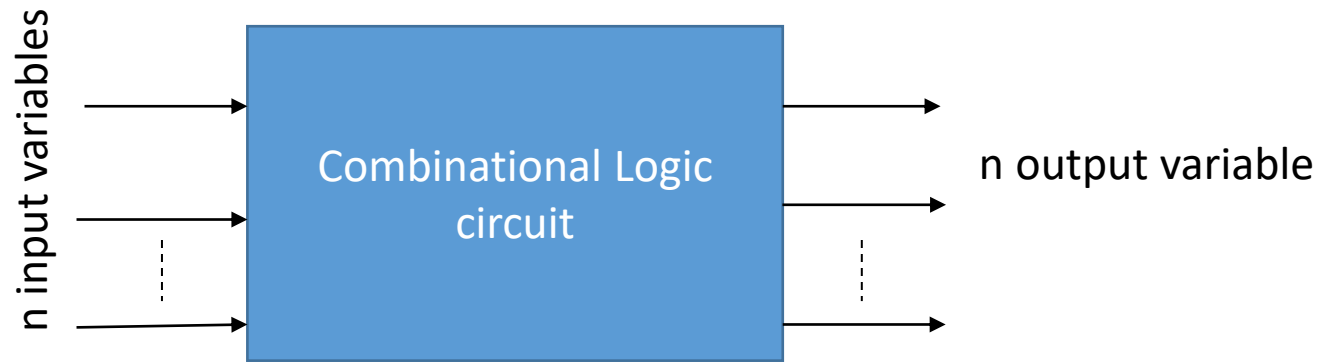


Fig 1. Combinational Logic Circuit

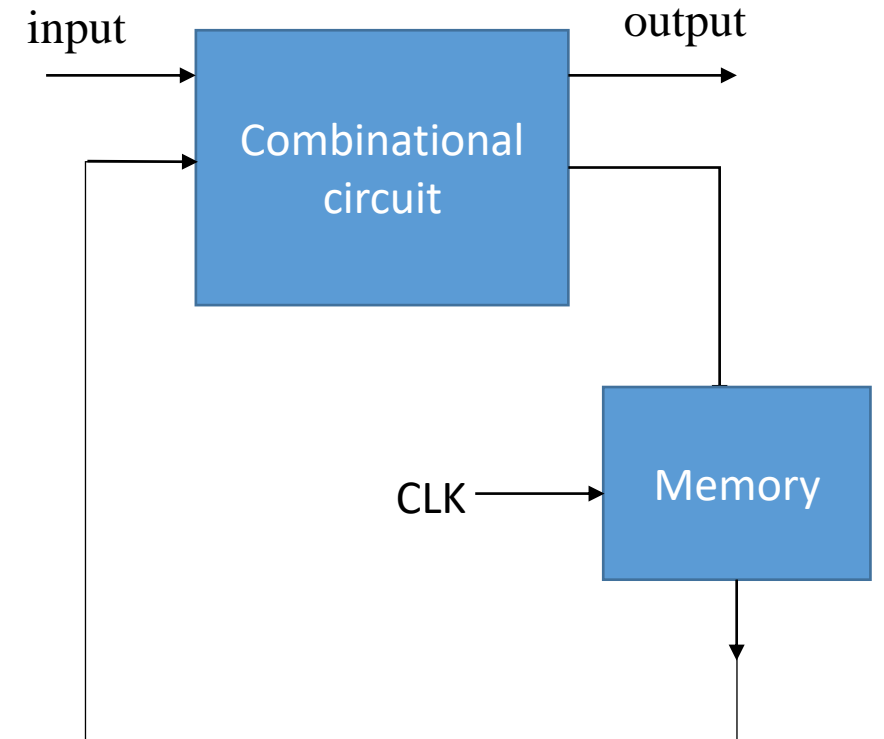


Fig 2. Sequential circuit

# Review of Sequential circuits

- Sequential circuits are commonly used in digital systems to implement state machines, timers, counters, and memory elements.
- The memory elements in sequential circuits can be implemented using flip-flops, which are circuits that store binary values and maintain their state even when the inputs change.
- *There are two types of sequential circuits:*
  1. *Asynchronous sequential circuit*
  2. *Synchronous sequential circuits.*
- *Asynchronous sequential circuit* **do not use a clock signal** but uses the pulses of the inputs.
- *Synchronous sequential circuits* These circuits **uses clock signal** and level inputs (or pulsed) (with restrictions on pulse width and circuit propagation).

# Flip-Flops vs Latch

- A FF is an electronic device that has two stable states. One state is assigned the logic 1 value and the other is the logic 0.
- These circuits are binary cells capable of storing one bit of information.
- A latch is a bistable circuit that is the fundamental building block of a flip-flop. It exists in one of the two states (e.g. 1 and 0), and in the absence of the input, it remains in that state.
- The following Fig. 3 illustrate a simple FF or 1 bit memory (i.e. it can store one bit of information  $y = 0$  or  $y = 1$ ) and since this information is locked or latched so, this FF is known as. a latch

 


Fig 3 : Simple Flip Flop or latch

# Flip-Flops

- *SR (Set-Reset ) Flip Flop 2ANDand2NOR*

**Case 1: S=0, R=0**

Gate1 = 0, Gate2 = 0, Gate3/Q(n+1) = Q, Gate4/Q(n+1)' = Q'

**Note:** Since one input of both gate3 and gate4 is 0 and both the gates are NOR gates the output of both the gates will complement the second input as per the property of NOR gates.

**Case 2: S=0, R=1**

Gate1 = 1, Gate2 = 0, Gate3/Q(n+1) = 0, Gate4/Q(n+1)' = 1

**Note:** Since one input of gate3 is 1 and gate3 is a NOR gate, output gate3 will be 0 irrespective of other input as per the property of NOR gate.

**Case 3: S=1, R=0**

Gate1 = 0, Gate2 = 1, Gate4/Q(n+1)' = 0, Gate3/Q(n+1) = 1

**Note:** Since one input of gate4 is 1 and gate4 is a NOR gate, output gate4 will be 0 irrespective of other input as per the property of NOR gate.

**Case 4: S=1, R=1**

Gate1 = 1, Gate2 = 1, Gate4/Q(n+1)' = 0, Gate3/Q(n+1) = 0

 


Fig 4 SR Flip-Flop

S	R	Q <sub>n+1</sub>	State
0	0	Q <sub>n</sub>	Hold
0	1	0	Reset
1	0	1	Set
1	1	X	Invalid

Fig 5 : Truth table of SR

# Characteristic Table and Boolean expression

Characteristic Table			
S	R	Q <sub>n</sub>	Q <sub>(n+1)</sub>
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	X
1	1	1	X

Fig 6 : Characteristic Table

K-Map  
→

S \ RQ <sub>n</sub>	R'Q <sub>n</sub> '	R'Q <sub>n</sub>	RQ <sub>n</sub>	RQ <sub>n</sub> '
	00	01	11	10
s' 0		1		
s 1	1	1	X	X

Fig 7 : K-Map

From the K-map we get 2 pairs. On solving both we get the following characteristic equation:

$$Q(n+1) = S + R'Q_n$$



# D FF(Works on output follows input principle)

 


Fig 8: D Flip-Flop

Q	D	Q(t+1)
0	0	0
0	1	1
1	0	0
1	1	1

Fig 9: Truth Table of D Flip-Flop

 


Fig 11 :Symbol of D FF

 


Fig 10: Characteristic Table

# JK-FF (It operates with only positive clock transitions or negative clock transitions)

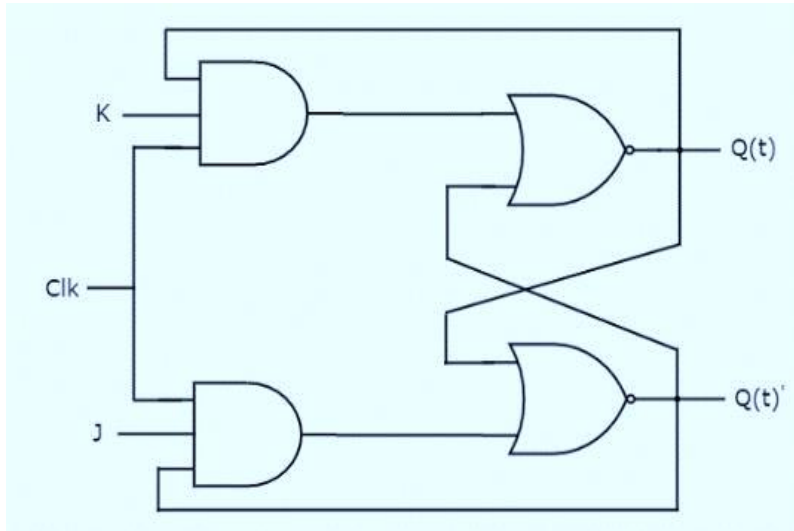


Fig 12: JK FF

J	K	$Q_{t+1}$
0	0	$Q_t$
0	1	0
1	0	1
1	1	$Q_t'$

Fig 13: State Table of JK FF

Present Inputs		Present State	Next State
J	K	$Q_t$	$Q_{t+1}$
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	0

Fig 14: Characteristic Table

 


Fig 15: K Map of JK FF

Simplified expression of K map is  $Q(t+1) = JQ(t)' + K'Q(t)$

**T-FF** (It is obtained by connecting the same input 'T' to both inputs of JK flip-flop. It operates with only positive clock transitions or negative clock transitions.)

 


Fig 16: T Flip-Flop

Inputs	Present State	Next State
T	$Q_t$	$Q_{t+1}$
0	0	0
0	1	1
1	0	1
1	1	0

Fig 18: Characteristic Table of T-FF

D	$Q_{t+1}$
0	$Q_t$
1	$Q_t'$

Fig 17 : State Table of T-FF


From the above characteristic table, By solving we can write the **next state equation** as

$$Q(t+1) = T'Q(t) + TQ(t)'$$


$$\Rightarrow Q(t+1) = T \oplus Q(t)$$
 
# Counters

- A counter is first described by a state diagram, which shows the sequence of states through which the counter advances when it is clocked.



 - The circuit has no inputs other than the clock pulse.
- No outputs other than its internal state (outputs are taken off each flip-flop in the counter).
- The next state of the counter depends entirely on its present state, and the state transition occurs every time the clock pulse occurs.



clk


- Once the sequential circuit is defined by the state diagram, the next step is to obtain the next-state table, which is derived from the state diagram

Present State			Next State		
Q2	Q1	Q0	Q2	Q1	Q0
0	0	0	0	0	1
0	0	1	0	1	0
0	1	0	0	1	1
0	1	1	1	0	0
1	0	0	1	0	1
1	0	1	1	1	0
1	1	0	1	1	1
1	1	1	0	0	0

- The number of distinct states the counter can take is  $2^N$ . It depends on the number of flip-flops that the counter has.

- There are two types of counting namely Up counting & Down counting
- In Up counting, If start the count with 0, the number of states will go to  $2^{N-1}$
- In Down counting, the count starts from  $2^{N-1}$  to 0.
- Let us assume that there are three flip-flops have the outputs A B C as QA QB and QC and the count starts from 0 0 0 then 0 0 1 .... 0 1 1.
- The complementary outputs (Q bar) Q'A Q'B and Q'C and this would start from 1 1 1, 1 1 0 .... 000.
- When take the output from Q, it becomes up counting as well as the output of Q' or Q bar becomes down counting.
- So it is a very major use of Flip-flops, (i.e.) use flip-flops in a chain and for counting events.
- If counter start from 000 to 111 and then again from 000, it is referred to full cycle.
- The total number of states the counter has is called MODULO or MODULUS.
- Sometimes, not want to count till the end of the last state or want to terminate the count at the count which is less than maximum and go back to 0.

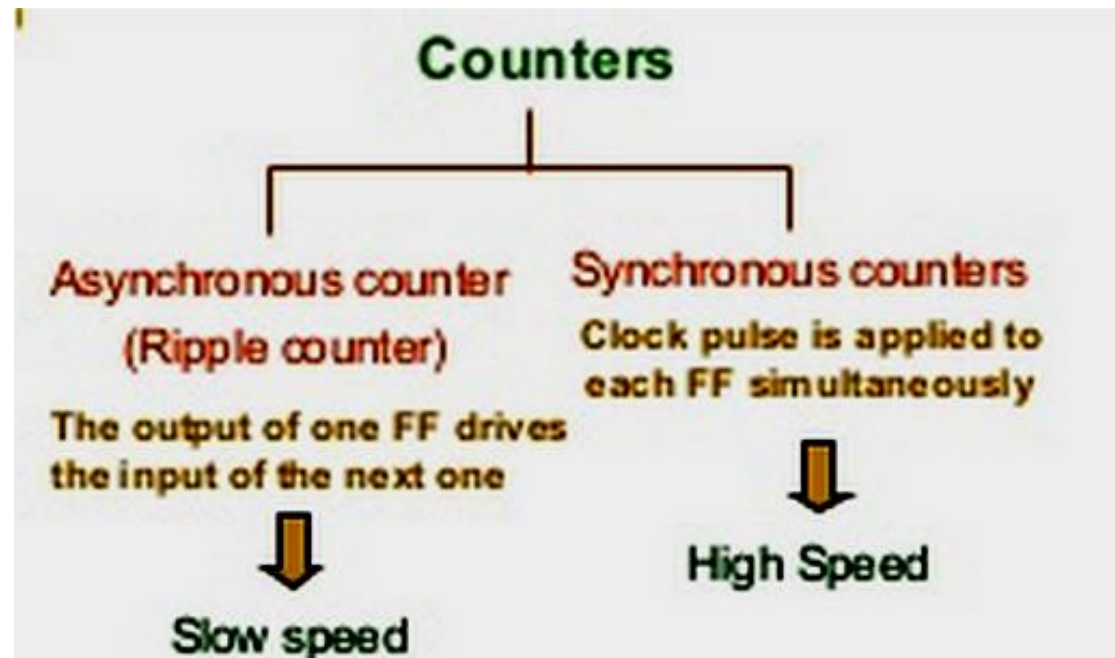- For example, the counter has four bits and it has 0 to 15 states and may want to terminate with 9 that is 0 to 9 and start again with 0, there will be a decimal counter.
- By using this decimal counter, able to start at any count or end at any count within the possible range.






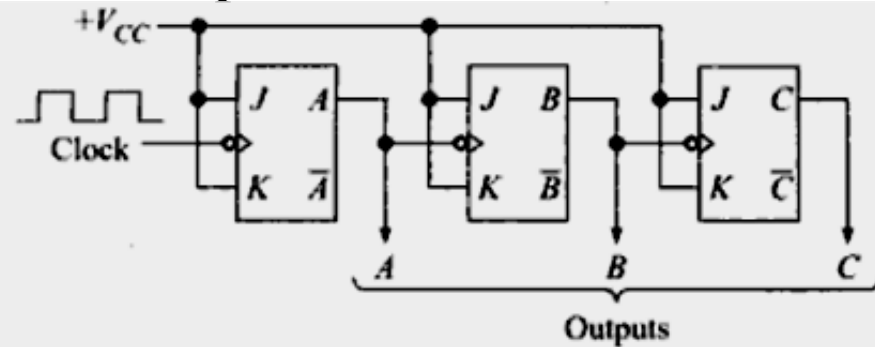
# Asynchronous (Ripple) Counters

- When the output of a flip-flop is used as the clock input for the next flip-flop, the counter is referred to as **ripple counter** or **asynchronous counter**.
- **Asynchronous counters**: the flip-flops do not change states at exactly the same time as they do not have a common clock pulse.
- In **ripple counters**, the input clock pulse “ripples” through the counter – the drawback is cumulative delay.
- A counter has a natural count of  $2^n$  where  $n$  is the number of FFs in the counter.
- Counter can operate in either a count-up or count-down mode.
- Digital clock is an typical application for counters.

- A binary ripple counter can be constructed using clocked JK FFs.
- The following figure shown Negative Edge Triggered, JK FFs connected in cascade.
- The system clock drives FF A. The output of A drives B, the output of B drives FF C.
- All the J & K inputs are tied to  $+V_{cc}$ . This means that each FF will change state with a NT at its clock input.



(a) Three-bit binary ripple counter

 


(b) Waveforms

Negative clock transitions	C	B	A	State or count
---	0	0	0	0
a	0	0	1	1
b	0	1	0	2
c	0	1	1	3
d	1	0	0	4
e	1	0	1	5
f	1	1	0	6
g	1	1	1	7
h	0	0	0	0


(c) Truth table
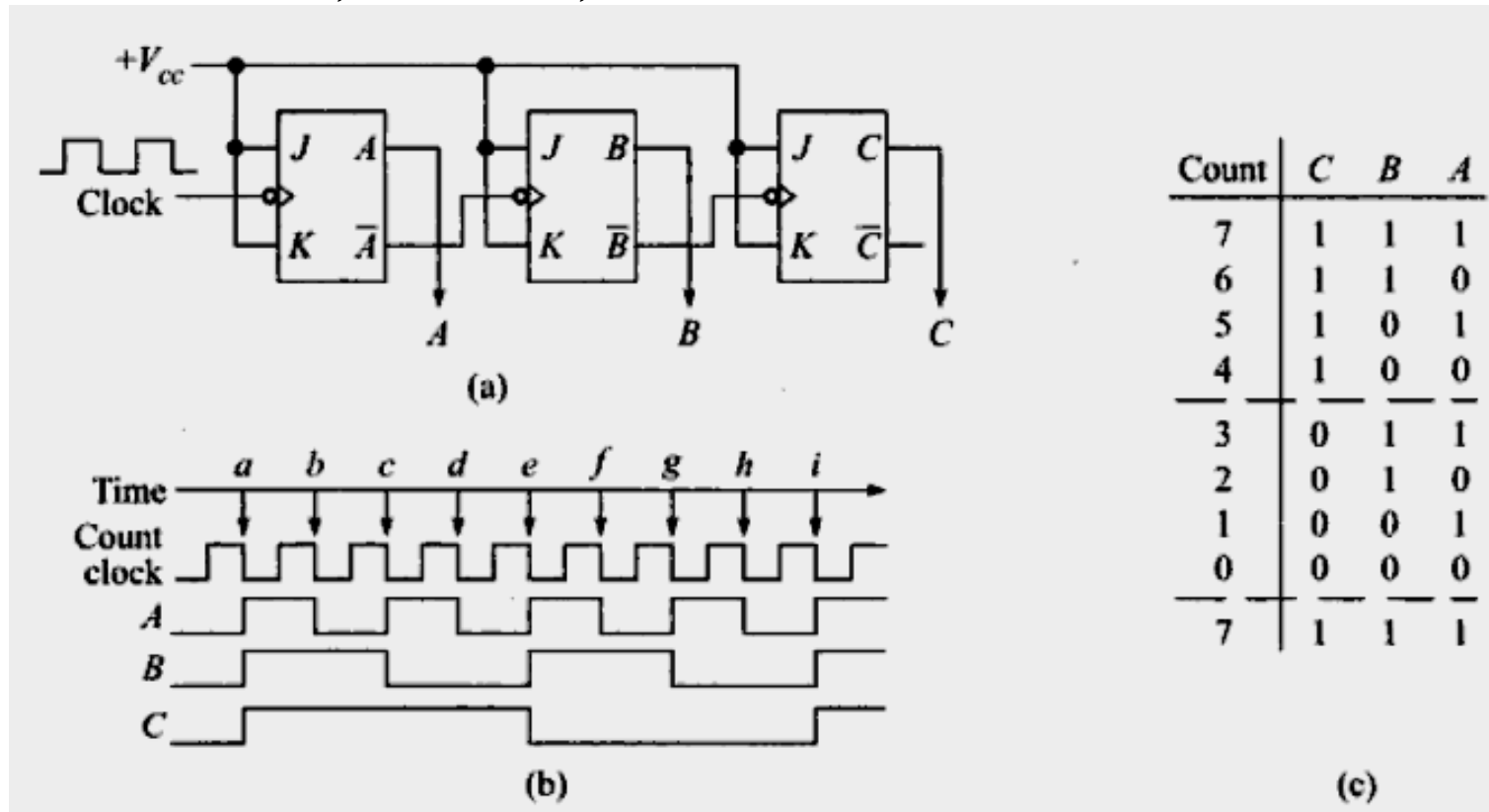
# Ripple Down Counter [3-bit ripple counter]

- The system clock is still used at the clock input to FF a, but the complement of A,  $A'$  is used to drive FF B, likewise,  $B'$  is used to drive FF C.




- A 3-bit asynchronous up-down counter that counts in a straight binary sequence is shown below.
- It is simply a combination of the two counters discussed previously.
- For this, counter to progress through a count-up sequence, it is necessary to trigger each FF with the true side of the previous FF (as opposed to the complement side).
- If the count-down control line is low and count-up control line high, and the counter will have count-up wave forms.
- On the other hand, if count-down is high and count-up is low, each FF will be triggered from the complement side of the previous FF.
- The counter will then be in a count-down mode and will progress through the waveforms.

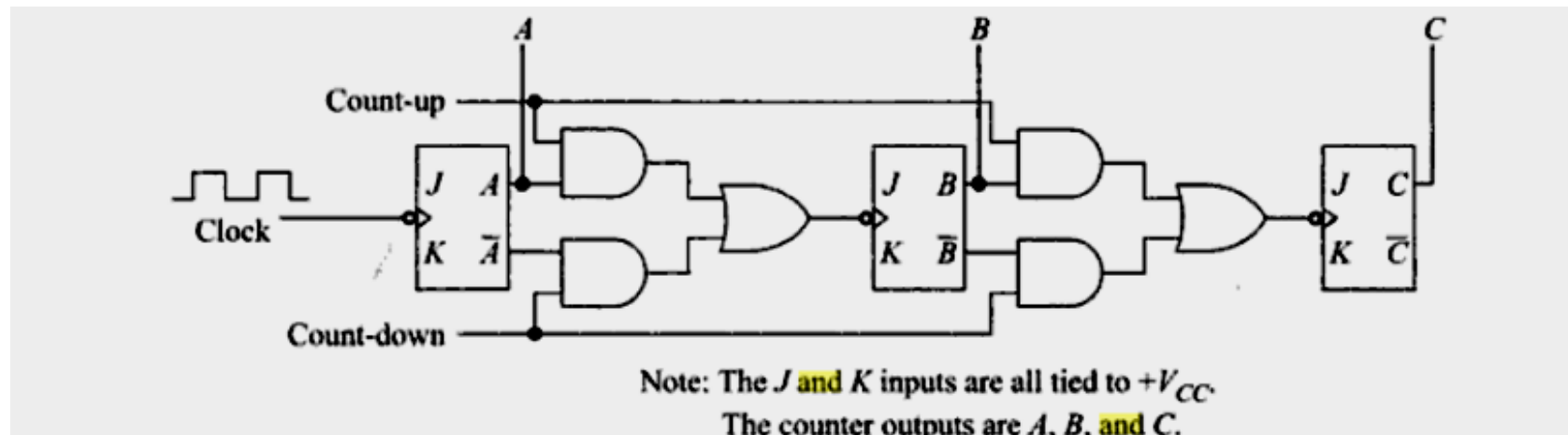

 
# Synchronous (Parallel) Counters

- Asynchronous counters are not useful at very high frequencies, especially for counters with large number of bits.
- Another problem caused by propagation delays in asynchronous counts occurs when try to electronically detect (decode) the counter outputs states.
- Both of these problems can be overcome by the use of a synchronous or parallel counter.

- **Synchronous (parallel) counters:** the clock inputs of all the flip-flops are connected together and are triggered by the input pulses.
- Clock pulses are applied to the input of all FFs.
- All the flip-flops change state simultaneously (in parallel).
- $T=0$  or  $J=K=0$  (FF does not change state)
- $T=1$  or  $J=K=1$  (FF complements)
- Design these counters using the sequential logic design process.
- Example: 2-bit synchronous binary counter (using T flip-flops, or JK flip-flops with identical J,K inputs).



Present state		Next state	
$A_1$	$A_0$	$A_1^+$	$A_0^+$
0	0	0	1
0	1	1	0
1	0	1	1
1	1	0	0

 

# References

- <chrome-extension://efaidnbnmnibpcajpcglclefindmkaj/https://ia600607.us.archive.org/3/items/DigitalLogicAndComputerDesignByM.MorrisMano2ndEdition/Digital%20Logic%20And%20Computer%20Design%20By%20M.%20Morris%20Mano%20%282nd%20Edition%29.pdf>
- <https://www.geeksforgeeks.org/introduction-of-sequential-circuits/>
- <https://www.electronicsforu.com/technology-trends/learn-electronics/sr-flip-flop-circuit-truth-table-limitations-applications>