

# Digital System Design EC 503

## Analysis and Synthesis of Asynchronous Sequential Circuits




Subject Coordinator  
Dr. GAURAV KUMAR BHARTI  
Department of ECE
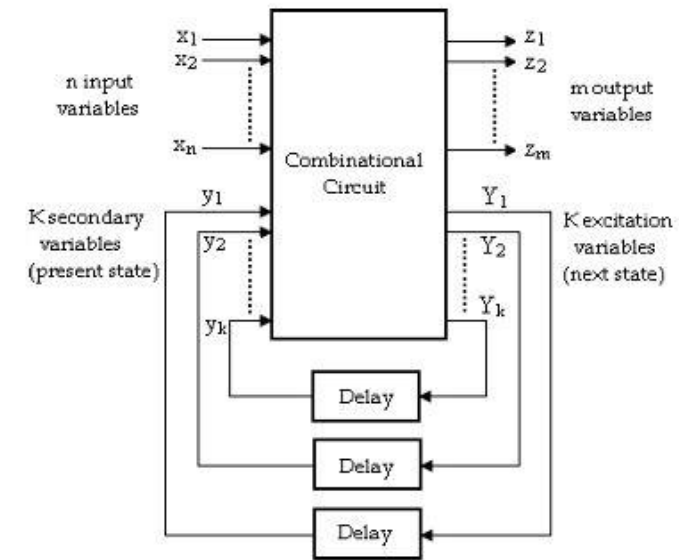
# Asynchronous sequential circuits



- Memory elements are either unclocked flip flops or time delay elements.
- The change in input signals can affect memory element at any instant of time.
- Because of the absence of clock, it can operate faster than synchronous circuits.
- Asynchronous sequential circuits do not use clock pulses.
- The memory elements in asynchronous sequential circuits are either unclocked flip-flops (Latches) or time-delay elements.



Block diagram of Asynchronous sequential circuits

- According to input variables there are two types

- Fundamental mode circuit

- The input variables change only when the circuit is stable. Only one input variable can change at a given time.
- Inputs are levels (0, 1) and not pulses.


- Pulse mode circuit

- The input variables are pulses (True, False) instead of levels.
- The width of the pulses is long enough for the circuit to respond to the input.
- The pulse width must not be so long that it is still present after the new state is reached.

- Analysis of Sequential Circuits

The analysis of Asynchronous sequential circuits consists of obtaining a table or a diagram that describes the sequence of internal states and outputs as a function of changes in the input variables.

# Analysis Procedure

 

Total State

Four stable total states –  $y_1y_2x = 000, 011, 110,$  and  $101$

Four unstable total states –  $001, 010, 111,$  and  $100$

Fig: Example of Asynchronous sequential circuit

 


Fig: Transition Table

- The transition table of asynchronous sequential circuit is similar to the state table used for synchronous circuits

	<b>x</b>	
	<b>0</b>	<b>1</b>
<b>y<sub>1</sub>y<sub>2</sub></b>		
<b>00</b>	<b>00</b>	<b>01</b>
<b>01</b>	<b>11</b>	<b>01</b>
<b>11</b>	<b>11</b>	<b>10</b>
<b>10</b>	<b>00</b>	<b>10</b>

<b>Present State</b>	<b>Next State</b>			
	<b>x = 0</b>		<b>x = 1</b>	
0 0	0	0	0	1

The procedure for obtaining a transition table from the given circuit diagram is as follows.

1. Determine all feedback loops in the circuit.
2. Designate the output of each feedback loop with variable  $Y_1$  and its corresponding inputs  $y_1, y_2, \dots, y_k$ , where  $k$  is the number of feedback loops in the circuit.
3. Derive the Boolean functions of all  $Y$ 's as a function of the external inputs and the  $y$ 's.
4. Plot each  $Y$  function in a map, using  $y$  variables for the rows and the external inputs for the columns.
5. Combine all the maps into one table showing the value of  $Y = Y_1, Y_2, \dots, Y_k$  inside each square.
6. Circle all stable states where  $Y = y$ . The resulting map is the transition table. Once the transition table is available, the behavior of the circuit can be analyzed by observing the state transition as a function of changes in the input variables.

# Flow Table

- During the design of asynchronous sequential circuits, it is more convenient to name the states by letter symbols than binary values.
- Such a table is called an flow table and is similar to a transition table, except that the internal states are symbolized with letters rather than binary numbers.
- The flow table also includes the output values of the circuit for each stable state.

$y, r$	0	1
$a$	$a$	$b$
$b$	$c$	$b$
$c$	$c$	$d$
$d$	$a$	$d$

(a) Four states with one input

$x_1, x_2$	00	01	11	10
$a$	$a, 0$	$a, 0$	$a, 0$	$b, 0$
$b$	$a, 0$	$a, 0$	$b, 1$	$b, 0$

(b) Two states with two inputs and one output



- If a transition table has only one stable state in each row then it is called as **primitive flow table**
- Figure (a) is called a primitive flow table because it has only one stable state in each row.
- Figure (b) shows a now table with more than one stable state in the same row.
- The binary value of the output variable is indicated inside the square next to the state symbol and is separated from the state symbol by a comma.
- To obtain the circuit described by a flow table, it is necessary to assign a distinct binary value to each state.
- Such an assignment converts the flow table into a transition table from which we can derive the logic diagram.
- Assign 0 to state a and 1 to state b, the result is the transition table
- The output map is obtained directly from the output values in the flow table

$y \backslash x_1 x_2$	00	01	11	10
0	0	0	0	1
1	0	0	1	1

(a) Transition table  
 $Y = x_1 x_2' + x_1 y$

$y \backslash x_1 x_2$	00	01	11	10
0	0	0	0	0
1	0	0	1	0

(b) Map for output  
 $z = x_1 x_2 y$



$$Y = x_1x'_2 + x_1y$$

$$z = x_1x_2y$$

 


Fig: Logic Diagram

# Race Conditions



- A race condition is said to exist in an asynchronous sequential circuit when two or more binary state variables change value in response to a change in an input variable.
- When unequal delays are encountered, a race condition may cause the state variables to change in an unpredictable manner.
- Races are classified as:
  - i. Non-critical races
  - ii. Critical races

# Non-critical races

- If the final stable state that the circuit reaches does not depend on the order in which the state variables change, the race is called a non-critical race.
- If a circuit, whose transition table starts with the total stable state  $y_1y_2x=000$  and then change the input from 0 to 1. The state variables must then change from 00 to 11, which define a race condition.
- The possible transitions are:

$00 \rightarrow 11$

$00 \rightarrow 01 \rightarrow 11$

$00 \rightarrow 10 \rightarrow 11$

In all cases, the final state is the same,

which results in a non-critical condition

 


Fig: Examples of Non-critical Races

- Races can be avoided by directing the circuit through intermediate unstable states with a unique state-variable change.
- When a circuit goes through a unique sequence of unstable states, it is said to have a cycle.
- Care must be taken when using a cycle that terminates with a stable state.
- If a cycle does not terminate with a stable state, the circuit will keep going from one unstable state to another, making the entire circuit unstable.

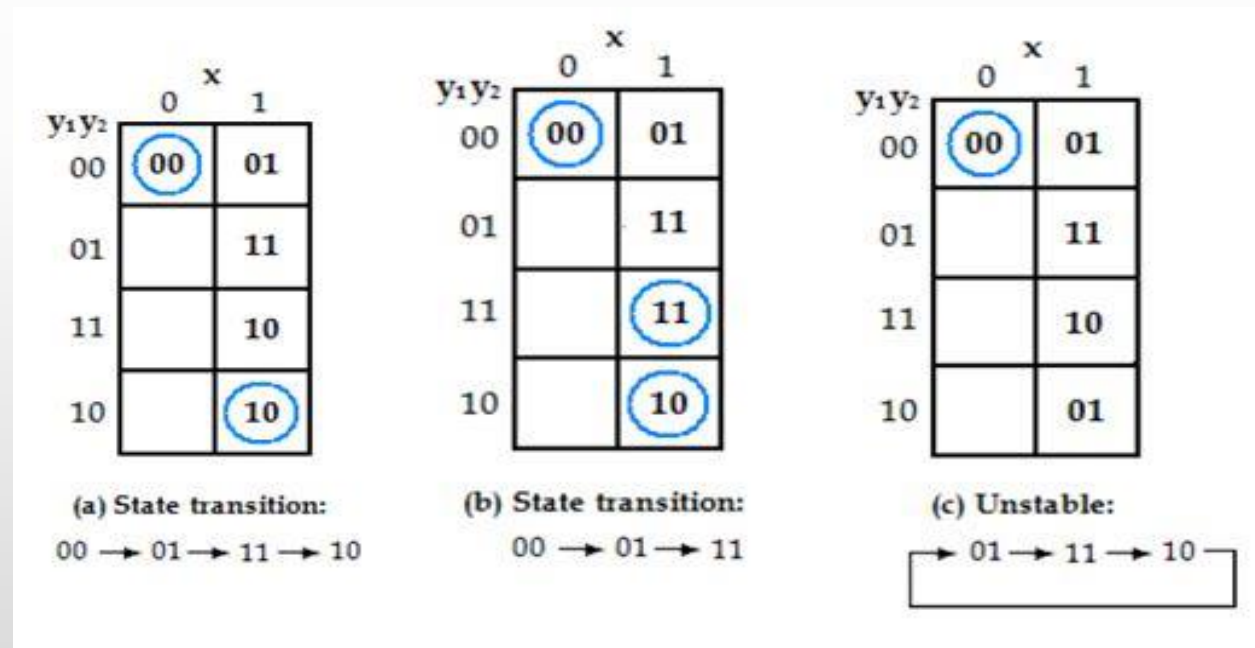


Fig: Examples of Cycles


# Hazards



- Hazards are unwanted switching transients that may appear at the output of a circuit because different paths exhibit different propagation delays
- Hazards occur in combinational circuits, where they may cause a temporary false-output value.
- When this condition occurs in asynchronous sequential circuits, it may result in a transition to a wrong stable state.
- **Hazards in Combinational Circuits**
- A hazard is a condition where a single variable change produces a momentary output change when no output change should occur.
- **Types of Hazards:**
  - Static Hazard
  - Dynamic hazard
- **Static Hazard**
- In digital systems, there are only two possible outputs, a '0' or a '1'. The hazard may produce a wrong '0' or a wrong '1'. Based on these observations, there are three types,
  - 1. Static- 0 hazard
  - 2. Static- 1 hazard
  - 3. Dynamic Hazard

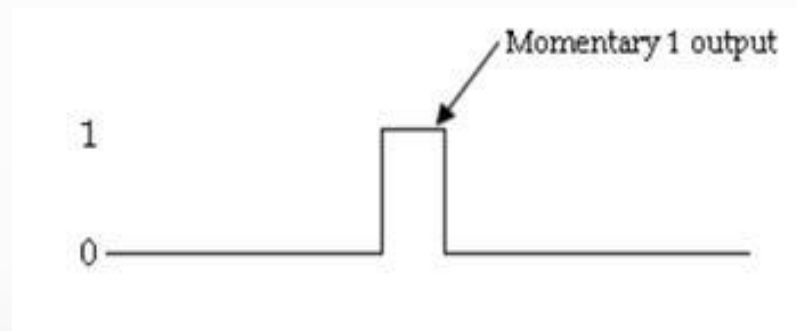
### ➤ Static- 0 hazard

- When the output of the circuit is to remain at 0, and a momentary 1 output is possible during the transmission between the two inputs, then the hazard is called a static 0-hazard.



### ➤ Static- 1 hazard

- When the output of the circuit is to remain at 1, and a momentary 0 output is possible during the transmission between the two inputs, then the hazard is called a static 1 hazard.

 

 


Fig: Circuit with static-1 hazard

 


Fig: Circuit with static-0 hazard




$X_1 \backslash X_2 X_3$	00	01	11	10
0	0	1	0	0
1	0	1	1	1

$$Y = X_1 X_2 + X_2' X_3$$

$X_1 \backslash X_2 X_3$	00	01	11	10
0	0	1	0	0
1	0	1	1	1

$$Y = X_1 X_2 + X_2' X_3 + X_1 X_3$$
 
### Maps demonstrating a Hazard and its Removal



**Hazard-free Circuit**

# Essential Hazard



- An essential hazard is caused by unequal delays along two or more paths that originate from the same input.
- An excessive delay through an inverter circuit in comparison to the delay associated with the feedback path may cause such a hazard.
- Essential hazards can be eliminated by adjusting the amount of delays in the affected path.
- To avoid essential hazards, each feedback loop must be handled with individual care to ensure that the delay in the feedback path is long enough compared with delays of other signals that originate from the input terminals.

# Thank You